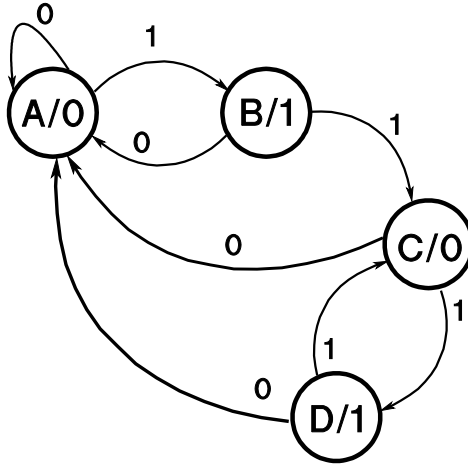



## CS150 - Computer Organization and Architecture

### Some Sequential Circuit Problems


1. Derive the state transition table, choose a state assignment, and write the next state and output equations for the following state diagram.



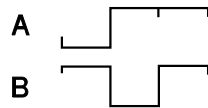2. Design a circuit which has one input  $X$  and two outputs  $A$  and  $B$ . When  $X$  is 0, the output should be:



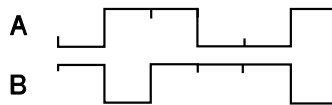When  $X$  is one, the above sequence should expand to



(That is, the second sequence is an “extension” of the first.)

3. Develop the *state diagram* for a variable counter circuit. This circuit has two inputs,  $A$  and  $B$ , two outputs  $X$  and  $Y$ , and should behave as follows:

- For  $AB = 00$ , the counter output should be 00 (i.e., stopped)
- For  $AB = 01$ , the counter output should be 00, 01, 00, 01, etc. (i.e., the counter should count to 1, then back to zero, etc.)
- For  $AB = 10$ , the counter output should be 00, 01, 10, 00, 01, 10, etc. (i.e., the counter should count up to 2, then back to zero)
- For  $AB = 11$ , the counter output should be 00, 01, 10, 11, 00, 01, 10, 11, etc. (i.e., the counter should count up to 3).

If the value of  $AB$  changes during a counting sequence, the counter output should go to 00 at the next clock cycle, and then count according to the new value of  $AB$ .

4. (This one is a more difficult problem!) Assume that a sequential network has two outputs  $Z_1$  and  $Z_2$ . The inputs  $(X_1X_0)$  represent a 2-bit binary number  $N$ . If the present value of  $N$  is greater than the previous value, then  $Z_1$  should be a 1. If the present value of  $N$  is less than the previous value, then  $Z_2$  should be a 1. Otherwise, both  $Z_1$  and  $Z_2$  should be zero, including the situation when the first value of  $N$  is received (in which case, we don't have a "previous value.") Draw the state graph for the circuit (*NOTE*: it is pretty large!).